

# ASSIGNMENT NO.6

Md Umaid Shaan

January 8, 2021

## 1 The Boolean Expression For "e"

$$e = A.\overline{B}.\overline{C}.\overline{D} + A.B.\overline{C}.\overline{D} + \overline{A}.\overline{B}.C.\overline{D} + A.\overline{B}.C.\overline{D} + A.B.C.\overline{D} + A.\overline{B}.\overline{C}.D$$

## 2 K-map Expression (simplified)

after simplifying the above boolean expression using k-maps it looks like this

$$e = \overline{A}.B + A.\overline{D} + \overline{B}.C$$

### 2.1 The Combinational Circuit

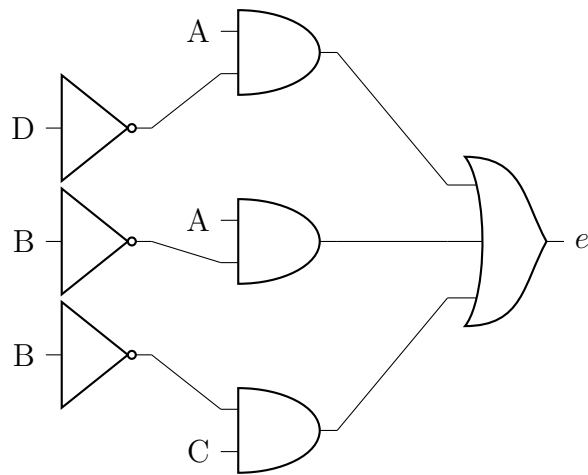


Figure 1: Circuit